




Textron Cooling Fan Project

Team: Electron Wranglers



Textron

- Ayham Sabra
 - EE
 - Project Lead
- Cody White
 - EE
 - Project Manager
- Mel St.John
 - EE
 - Scribe
- We are going to monitor and make sure a BLDC motor stays within our threshold RPM



Ayham Sabra: Environmental/Component Requirements

- The Environmental Requirements we have are
 - Make sure it works in -55 to 85 Celsius
 - Must be able to operate in altitudes from -1,000 ft to 55,000 ft
 - Make sure it follows DO 160G sections 6, 8 and 22
 - Humidity, Vibration and indirect effects of lighting
- I have contact Textron, the library and NAIR for a copy DO-160G
 - Textron will show us a there copy once we have finished a prototype with all other parts they're looking for
 - Haven't gotten a response for NAIR


Cody White Input



- Receives a power input of 28 V of DC power, but must operate from 10 to 80 V.
- Receives a tachometer input that operates from 0 to 5 V or 0 to 28 V.
 - The Tachometer input is a square wave.
 - Should be able to accept frequencies from 0 to 1 kHz.



<https://www.3ccooler.com/cooler-master-12025-a12025-20rb-3bn-f1-df1202512rfun-r4-l2r-20ac-gp-12v-0-37a-3-wires-led-cooler-fan.html#product-details-tab-specification>

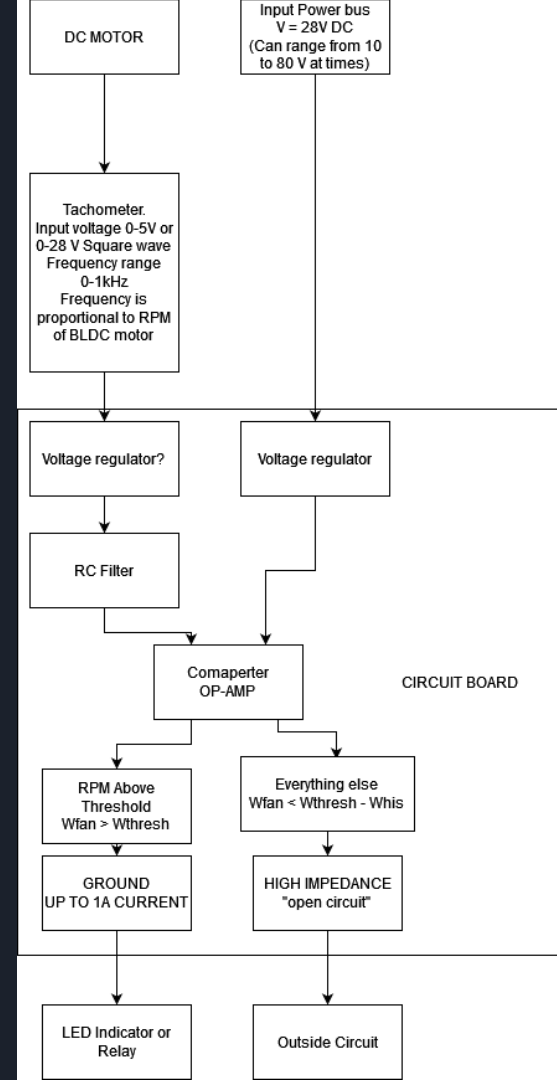Source for fan photograph. This is the same fan provided by Textron for testing,




Cody White

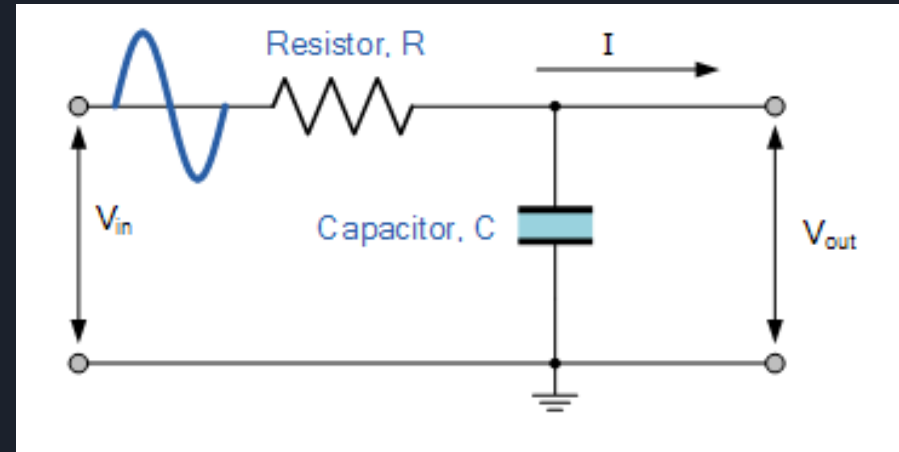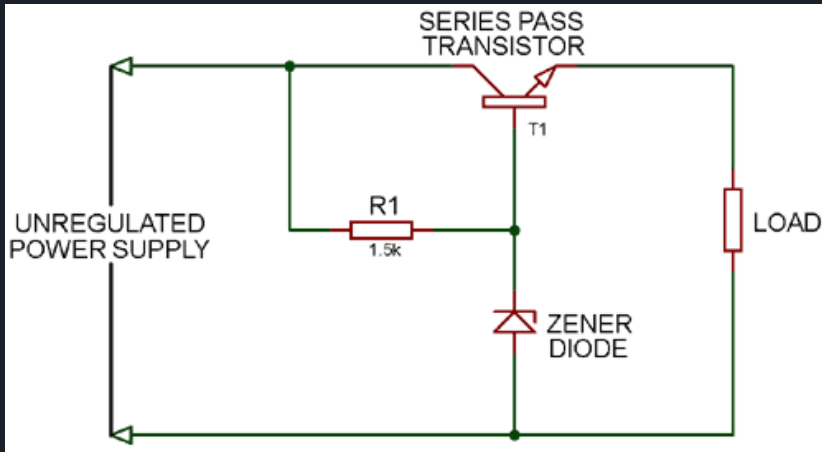- Based on research into RC filters, we have determined we'll need a low pass filter for the tachometer output to create a smooth signal.
- Based on research into voltage regulators, we have determined we'll need a passive voltage regulator to lower the input coming from the power bus.




Mel St.John Output

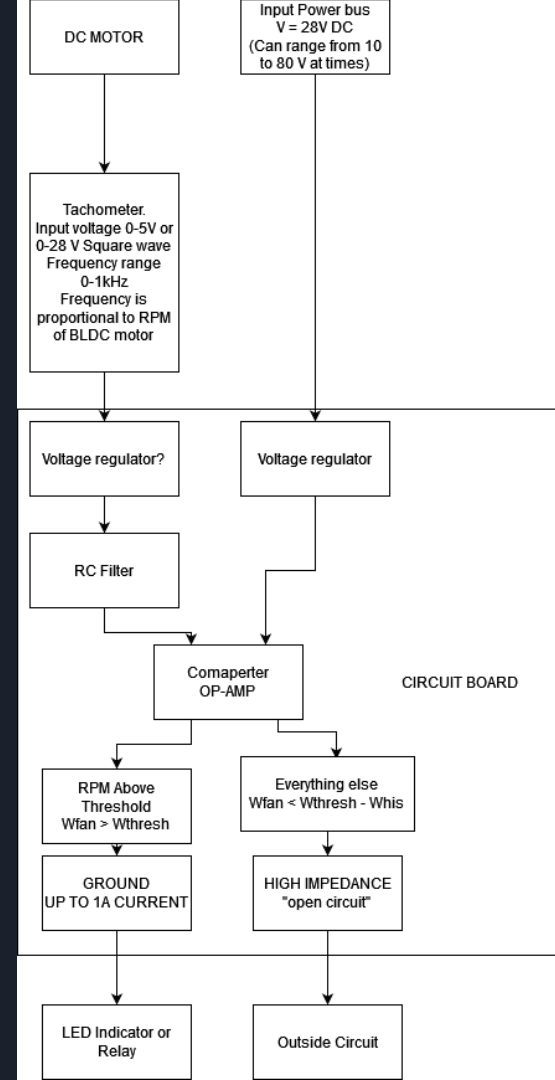- Component Constraints
 - Make sure to not use programmable chips (No memory in chips)
 - Other testing required for these chips (DO-178 and/or DO-254)
 - Make sure components are generic and can't easily go obsolete
- O/P goes to ground if Rpm above threshold
- O/P provides an open if Rpm below threshold
- Sink 1 amp continuously when providing ground
- Should incorporate hysteresis





Mel St.John

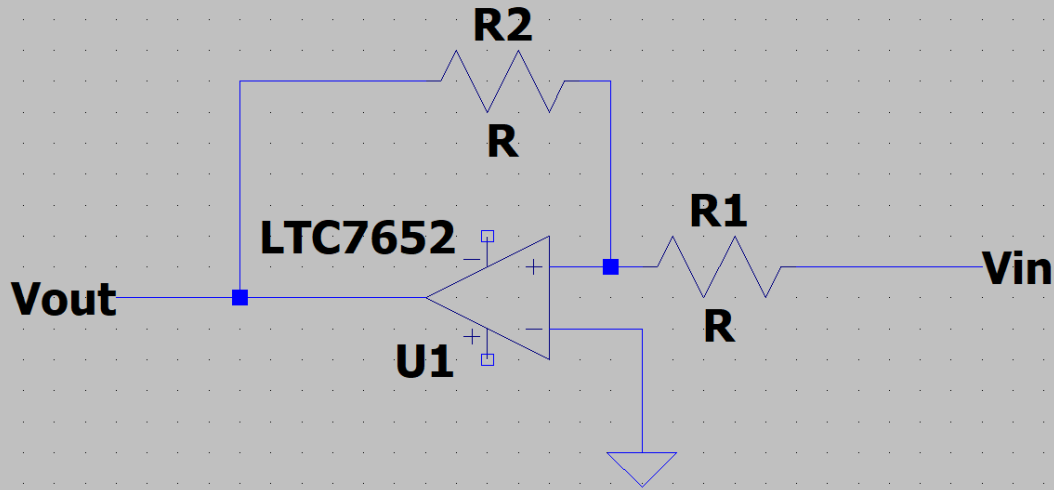Comparator- Schmitt Trigger (with Hysteresis Feedback)




Ayham Sabra

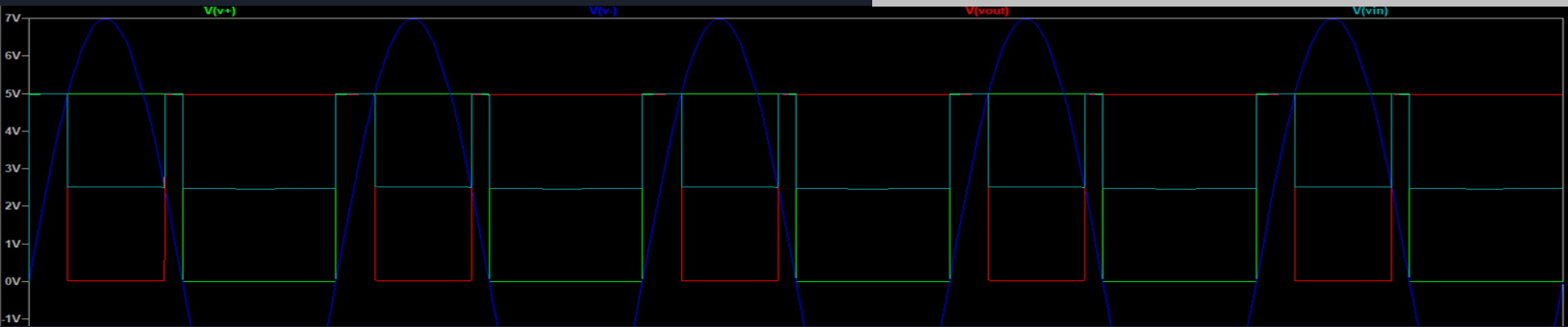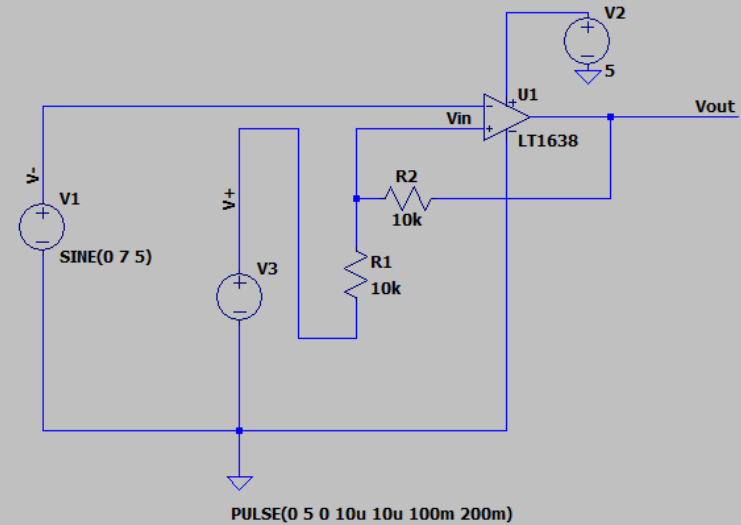- Schmitt Trigger Comparator Circuit in LTspice




Ayham Sabra


- Fan Tachometer measurements

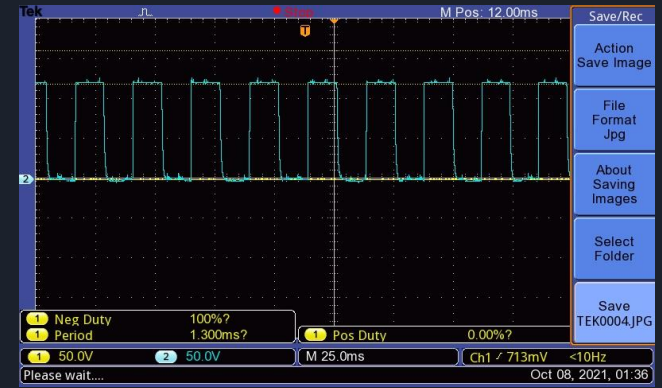

Slowed down

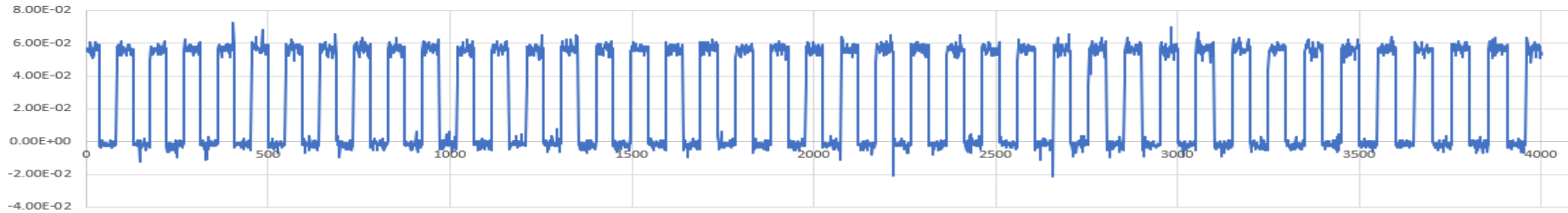

Not slowed

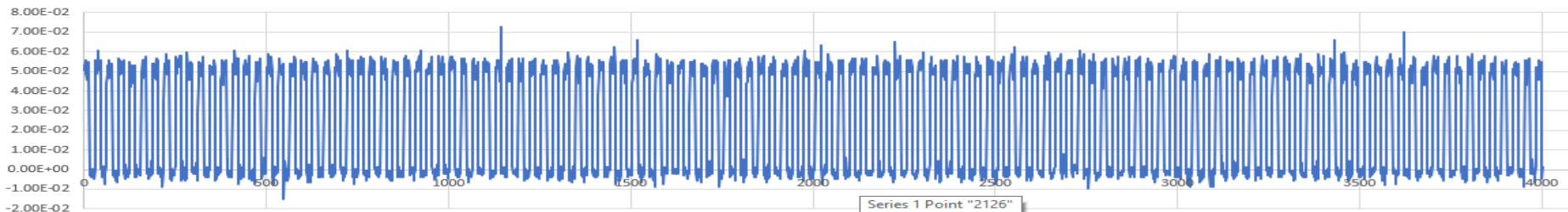



Thank you